

c005

C005 Cheap Delay Timer


Need to turn off your circuit for some time but don't want to fiddle with a microcontroller/sleep settings? How about using a delay timer board for 10 cents?



•
•


Benjamin Lim

Aug 24, 2019 • 5 min read

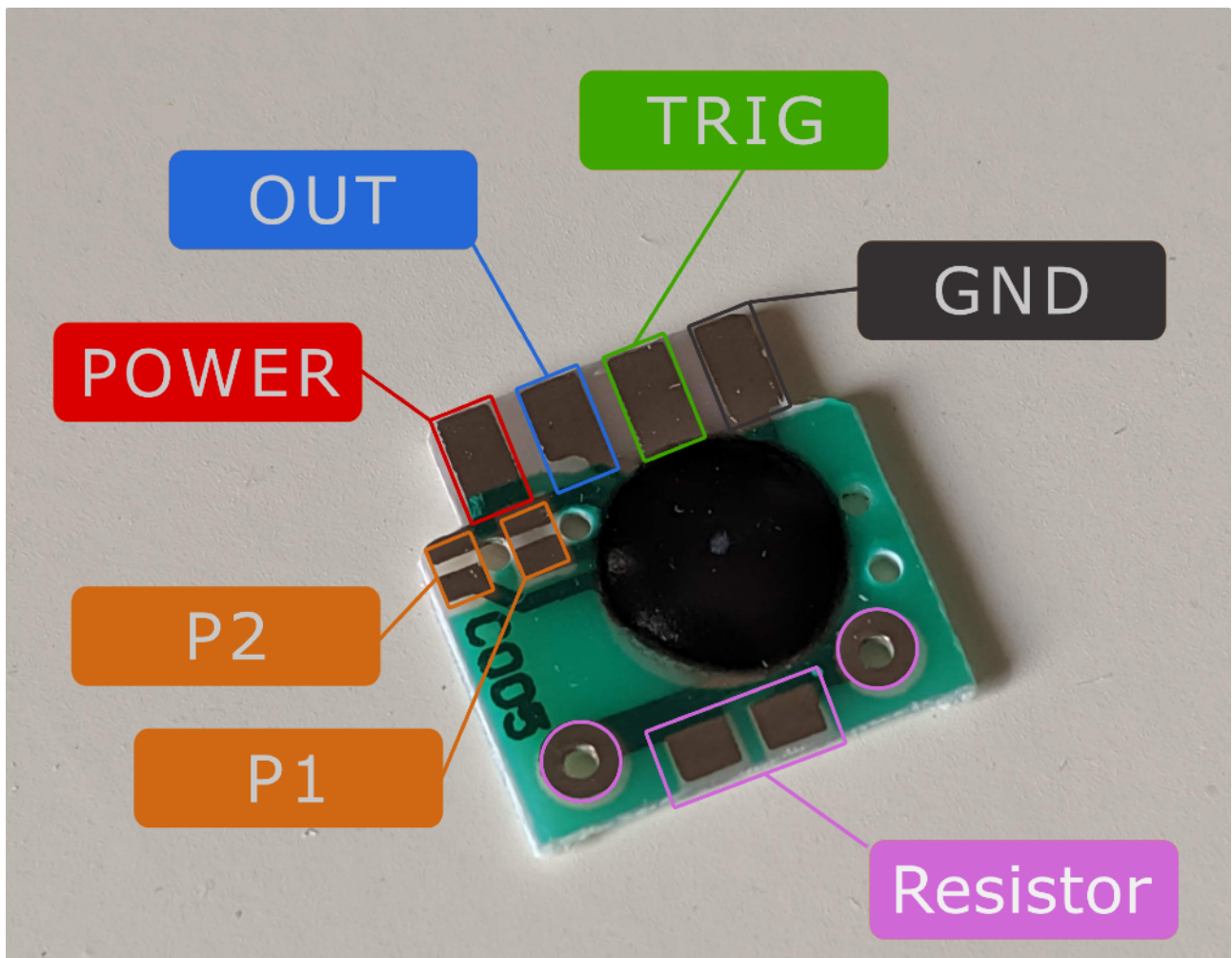

I recently got very interested in controlling the amount of power my boards use because between transmitting data and using battery powered devices, there isn't a whole lot of energy to spare if you don't want to be tied to a wall wart.

Adafruit and Sparkfun both sell the TPL5110 breakout boards that essentially act as delay switches that start a timer when a switch closes. The system shuts off the power by sending a signal to the trigger pin, which opens the circuit. When the period is up, the switch will open again. However, because it is a little expensive for me, I was looking around for alternatives, and this little board caught my eye:

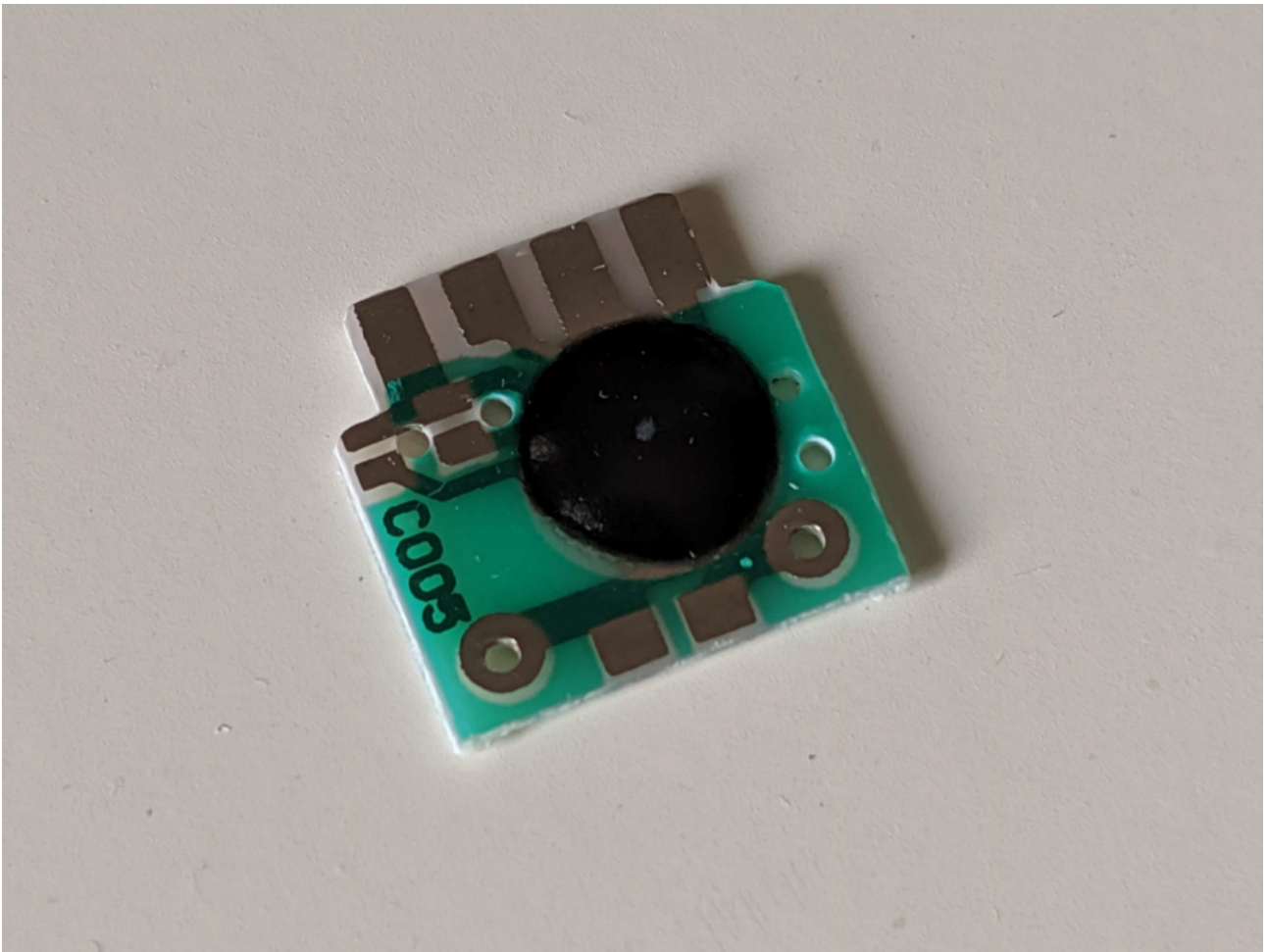

This is advertised as *delay timing chip/delay chip/ Trigger delay IC/2s-1000h timing IC*. It is also known as the C005 delay chip due to the markings on the side. It is literally a piece of PCB with an epoxy glob. It also costs about 50 times less than an equivalent board from Adafruit or Sparkfun. Unfortunately, all of the descriptions online appear to be a copy-paste of the original instructions, which is a set of gibberish sentences in English:

Specifications:

Shape about 12mm * 12mm, operating voltage 2v-5v, timing can be set to a minimum to a maximum of 2 seconds 1,000 hours, as indicated below description

Function and Design

1. The circuit according to claim connected and set a good time resistance and supply voltage;
2. Before the power not trigger output is high;
3. Trigger terminal "falling" trigger effective immediately after the trigger output terminal goes low at the same time start the timer circuit;
4. Set the timer time to recover after the output terminal is high, wait for the next "falling" trigger;
5. The chip is not repeated triggered, meaning that continue to trigger in the period after the trigger chip output low if the trigger is invalid;
6. The trigger end of "falling" Trigger refers to the instantaneous change from high level to a low level;
7. General refers to VCC high voltage, low means 0-0.3v or GND, provided that they meet the level requirements can be;
8. trigger terminal can be connected to touch switch or microcontroller IO port or other digital circuits have a "falling" can effectively trigger;
9. The trigger can be designed to power, only to trigger a short circuit to ground, power is triggered, the time to recover after the output to a high level, waiting for the next Falling edge trigger again.

Chip Features:

1. The use of low-power CMOS technology, lead-free and environmentally friendly.
2. Direct Push can output low LED (please add current limiting resistor), the output high may push transistor (please add current limiting resistor).
3. Available resistance adjusting timing, there are 8 * N (N = 0.1.2.3) times the timing selection, time can be adjusted from 2s-1000h.
4. Optional trigger timing and triggering termination ground electric timer.
5. standby output high, falling edge trigger, post-trigger output low, after the delay recovery high.

Hard to understand!

Translation

Specifications

The size of the board is 12mm x 12mm, with an operating voltage of 2v to 5v. The timing that the Output is low for can be set to a minimum of 2 seconds and a maximum of 1000 hours.

Function


1. While the trigger is not activated the output is high. The trigger can be activated by sending a falling signal to the trigger pin.

2. Once the trigger is set by an external controller, the output goes low. An internal timer starts as well.
3. Once the timer completes, the output will reset and the chip will wait for the next falling signal.
4. The chip is not repeatedly triggered, meaning that in the time between it is triggered and resets, it will not respond or keep track of any other falling signals from the external controller.
5. The trigger can be tied to the output as a short detector, so it will cut off the power when there is a short circuit to ground. It will then attempt to reset the power after a short period of time. (a pretty nifty feature!)

Features

1. Uses CMOS and is lead free (this is debatable)
2. It can be used to power a LED or may be used to control a transistor that can be used as a switch for high-power circuits. Current limiting resistors are required.
3. The timing can be changed by adjusting the resistance, and there are prescalers available to further change the timing.

Diagram

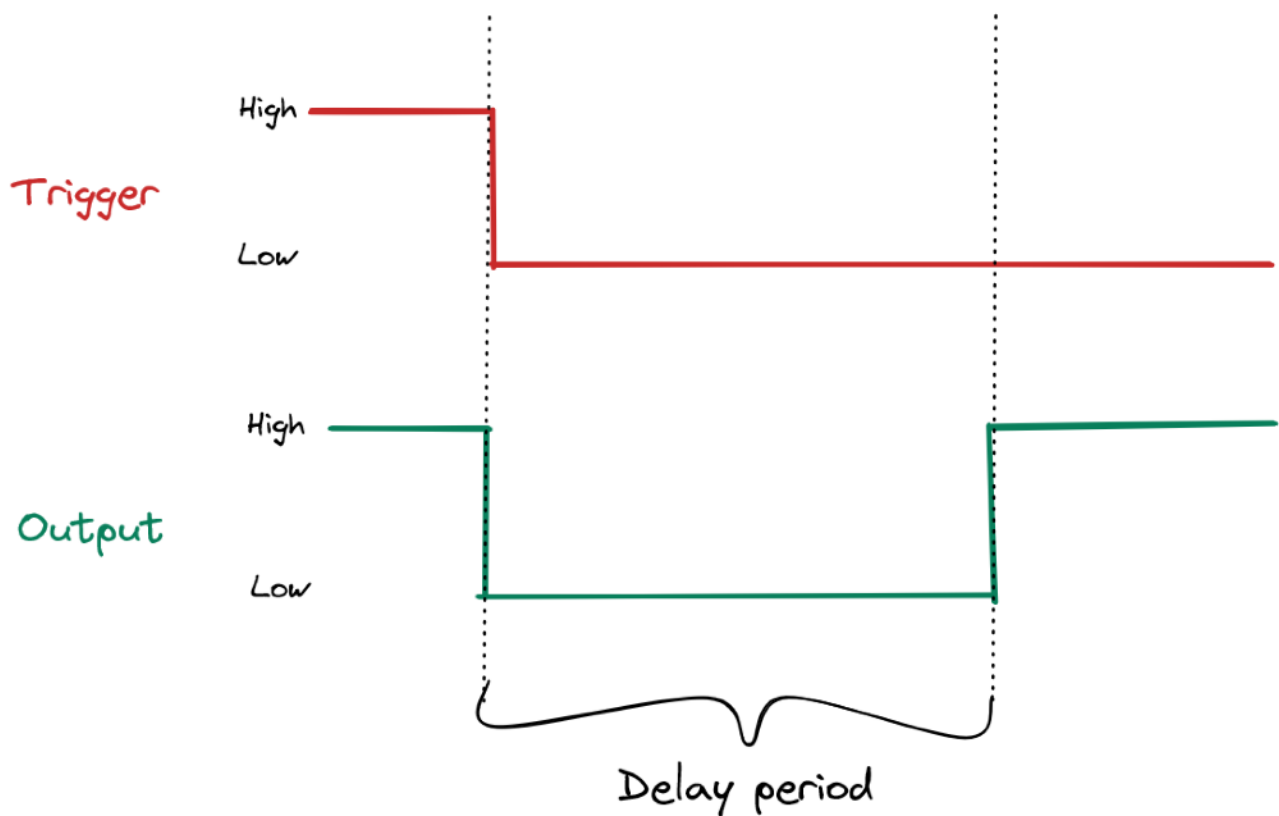

Testing

After some experimentation with the C005 IC, I figured out that when `Trigger` is pulled to `LOW`, the falling edge causes the `OUT` pin to go `LOW` for a specific period of time before going back to its default state of `HIGH`.

This is a one shot timer because it requires an external input for it to change state.


For a low power circuit, the ground can be tied to the `OUT` pin. This way the delay works as a low side switch and controls power to the circuit through the connection to ground. If an external trigger is activated, the circuit will turn on and process the event for a predetermined length of time before it turns off.

Another way this can be used is to tie the output to a transistor that acts as a high power switch. Let's say I want a circuit to turn off for an hour each time. I will first pick out a resistor that gives me an hour from the timing table, then I will then program my microcontroller to send a signal to the trigger pin when it is done. This will cause the output to go low for the specified period of time (an hour) before it automatically goes back to high again.

The 0UT pin is not able to source a significant amount of current, so it is not possible to run a circuit directly from the 0UT pin unless your current requirements are very small. Holding the Trigger down does not automatically trigger the output again, as the condition for toggling the 0UT pin is a falling edge on the Trigger pin.

The nice thing about this chip is that the solder pads are spaced 0.1 in apart, so they can be soldered to standard headers. Another benefit of this IC is that it can also be used as a timer for a much longer period than the TPL5110. While it definitely does take up more space, it is 10x cheaper than a TPL5110 in single quantities, costing about \$0.15. I measured the timing period to be stable to a few milliseconds.

Connecting the circuit

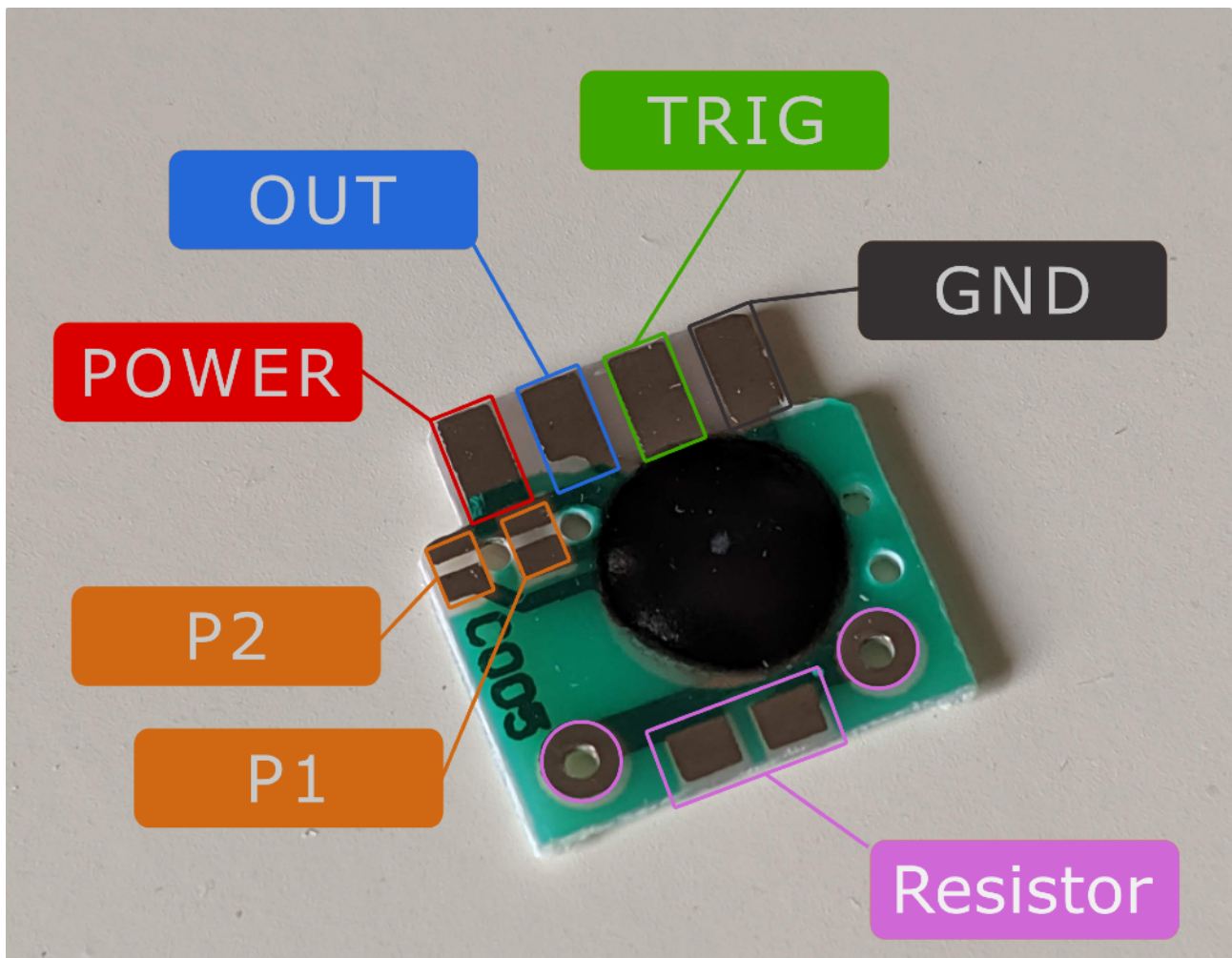

C005 overlay, made in Inkscape

This chip takes in voltages from 2V to 5V. You will need to solder a resistor to set the timer.

P1 and P2 are primarily used to extend the time. By shorting P1, you extend the time by 8 times, by shorting P2, you extend the time by 64 times. Shorting both yields a time extension of 512 times.

By placing either a SMD resistor or a through-hole resistor on the board, the time can be varied as seen in the reference table at the bottom of the post. The timing is also dependent on the voltage that is applied to the circuit. Alternatively, you can also add a trimpot to vary the delay.

For stability, a pull-up resistor can be added to the trigger pin. Do note that the output pin appears to be capable of sinking up to 30mA and is not a full power

switch. You will need to add the power circuitry yourself if you intend to use this timer IC for high powered operations.

Steps

1. Select a resistor and solder it in
2. Connect power and ground
3. Tie the trigger pin to an external device or switch
4. Tie the output pin to the circuit to be powered

Power consumption

This chip/board draws about 100uA when active (when it is keeping time, **OUT** is low). It draws about 1uA when it is sleeping. It does not provide much benefit compared to sleep modes, which for the nRF52840 or ESP32, draws about a few uA when they are sleeping. However, if we are considering a more complex circuit like a board with other components that are also drawing power, then maybe this chip has a role in being the middleman for power management. This can also be useful in circuits that need to be timed but don't have a microcontroller, or retrofitting existing circuits to have sleep features.

Reference Table

These times apply when both P1 and P2 are not shorted.

RESISTANCE	TIMING UNDER 3V (S)	TIMING UNDER 4.5V (S)
10K	5.8	4.8
20K	8.9	8
30K	12.1	11.4
51K	19.2	18

75K	26.5		25
100K		34	32
150K		49	46
200K		65	60
240K		78	74
300K		96	92
390K		123	119
510K		155	150
560K		175	168
620K		199	187
750K		230	222
820K		255	246
1M		330	291
1.5M		383	432
2M		598	568
3M		762	762
4.7M		1425	1165
5.1M		1631	1331
10M		2921	2621
15M		4394	3813
20M		5160	4660
22M		7052	6452